

# Switches

Electricity All Around Us  
Learner Worksheet  
Grade Level: 5-8



Group Member Names:

## Switch One

1. Draw your group's first switch design. Label the parts.

2. List your observations of the first switch.

---

---

---

---

---

---

3. How does your switch work?

---

---


4. Where would a switch like this be useful?

---

---

### Switch Two

 5. Draw your group's second switch design. Label the parts.



6. List your observations of the second switch.

---

---

---

---

---

**7. How does your switch work?**

---

---

**8. Where would a switch like this be useful?**

---

---

**Questions**

**9. If we did not have switches, what would be different in our lives?**

---

---

---

**10. List 10 items that use switches to operate.**

---

---

---

---

---

---

---

---

---

---

---