

Making Fuses

Electricity All Around Us
Learner Worksheet
Grade Level: 5-8



Group Member Names:

Observation Sheet

1. Draw your group's circuit with the fuse. Label all the parts.

2. What happened to the fuse when you connected the wire?

3. What is the purpose of a fuse?

4. Fuses have been replaced by circuit breakers. List some reasons for switching from fuses to circuit breakers.
