

Lighting a Light Bulb

Electricity All Around Us
Activity
Grade Level: 5-8



Main Objectives

Learners will design and construct circuits that operate lights and other electrical devices.

Learning Outcomes

By the end of this activity, learners will:

- Arrange materials to construct a circuit
- Understand the components of a circuit

Length of Activity

1.5 hours

Materials List

Internet-enabled device
Lighting a Light Bulb Backgrounder
Lighting a Light Bulb Learner Worksheet
Battery (1.5 V)
Wire
Small bulb
Tape
Wire strippers

Before you begin:

Read the Lighting a Light Bulb Backgrounder to find some useful tips on how to get your light bulb to light up. Then use the materials listed above to create a closed circuit and light up your light bulb. Record information on your worksheet and do the activity.

Visit [Brain pop!](#) for video clips of electricity and how it works.

Activity

Step 1:

- a. Review the information provided in the Lighting a Light Bulb Backgrounder.

Step 2:

- a. Explain to the learners that they will be using materials to light up a light bulb. Instruct the learners that there needs to be a connection at the metal tip and at the metal contact of the bulb for it to light up.
- b. In small groups or individually, have the learners try to make the light bulb light up and complete the worksheet.

Tips and Extensions

- To ensure the success in the experiment, test the batteries and use only well-charged batteries.
- Be aware of the voltage needed to light up a light bulb. Check to see if the light bulbs being used can be used with the batteries chosen.
- Use wire strippers to expose the end of the wire by removing any insulating materials. Copper wire is coated with a thin amount of lacquer, which can be taken off by brushing the wire with sandpaper.
- Use a solar cell, alligator clips, a motor and propeller. Attach the alligator clips to the solar cell and then to the motor with the propeller.

- Place the cell under a direct light source to produce enough energy to make the motor spin the propeller.

Comprehension

- Can you trace the path of the current?
- Is there more than one way to make the light bulb light up?
- Did you or your group try different things? What worked? What did not? Why do you think that happened?